

Electricity

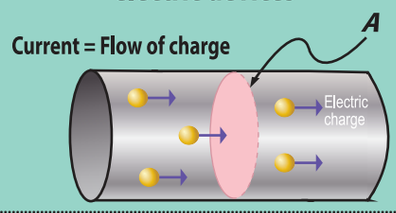Electric current is the flow of electric charges, typically through wires, conductors and electric devices



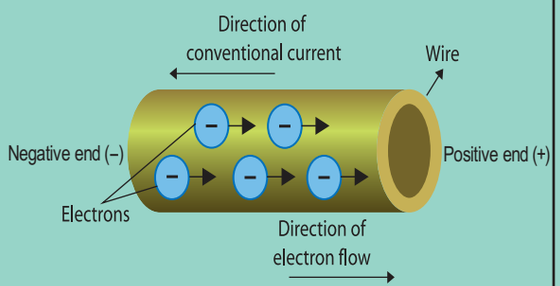Conventional current and Electric current



Conventional current

Conventional current flow is from positive (`+`) to negative (`-`)


Electric current

Electric current flow is from (`-`)negative to (`+`) positive

Electric current I = Q/t


Water current vs electric current - Analogy

Water current in a river

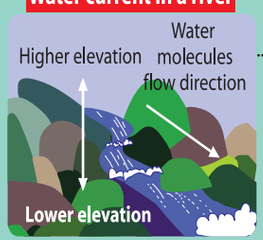


water molecules flow towards a point of lower elevation

Electric current in a wire

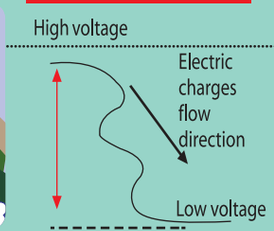


Electric charges flow towards a point of lower voltage

Open circuit

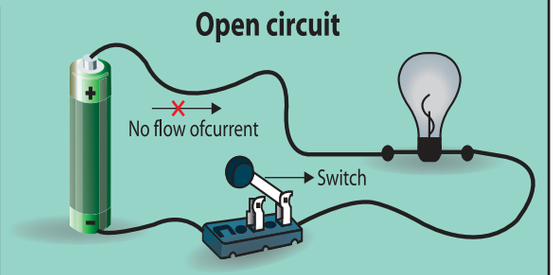


An incomplete electrical circuit in which no current flows

Closed circuit

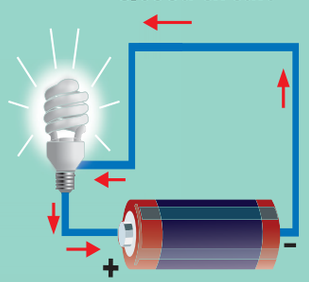


An electric circuit providing an uninterrupted endless path for the flow of current

Series circuit

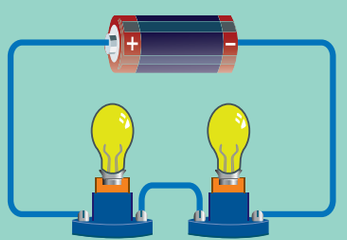

Circuit that has only one closed path through which the electric current flows

Parallel circuit

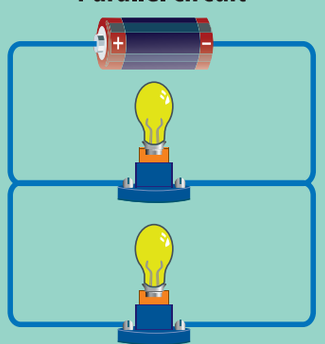

Circuit that Offers more than one path for the flow of electric current

VII Std Science Term-2 EM Unit 2.indd 24 7/15/2022 2:35:15 PM