
ICT CORNER

ELECTRICITY

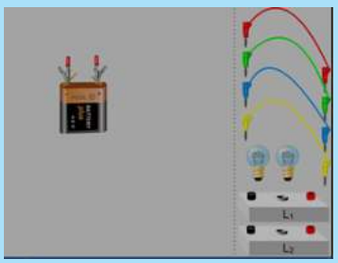This activity helps the students to understand about the Parrellel and series circuit



PROCEDURE :

Step 1: Type the URL link given below in the browser or scan the QR code. A page opens with a battery , some cables, two sets for circuit and two bulbs.

Step 2: Ask the students to fix the wires to the battery and the circuit


Step 3: Let the students do it and understand the concept with different combinations



Step 1



Step 2

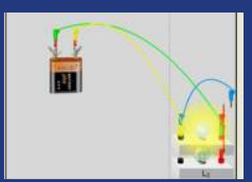

Step 3

Electricity URL:

http://www.physics-chemistry-interactive-flash-animation.com/electricity_electromagnetism_interactive/components_circuits_association-series_parallel.htm

*Pictures are indicative only

*If browser requires, allow Flash Player or Java Script to load the page.

T8YRD

VII Std Science Term-2 EM Unit 2.indd 35 7/15/2022 2:35:20 PM